



Application Note


Effect of Gate-Emitter Capacitor C_{GE}

Attached you find some informations, which should give explanations about the advantages of using an additional gate capacitor C_G .

The main idea behind this is to control di_C/dt and dV_{CE}/dt **independently** at **turn-on**. The need for this is given by the wish for lowest IGBT turn-on losses and a not unlimited di/dt -capability of the free wheeling diode.

By just raising the R_G (until the di_C/dt_{max} is ok) would increase the turn-on losses E_{on} . With the additional component C_G the di_C/dt can be controlled by the time constant given by R_G and $C_{GE} // C_G$. For the turn-on dV_{CE}/dt only R_G and $C_G // C_{GC}$ (C_{GC} : Miller-capacity) are effective. Because $C_{GC} \gg C_G$, finally only R_G (and not C_G) is responsible for the resulting dV_{CE}/dt value !

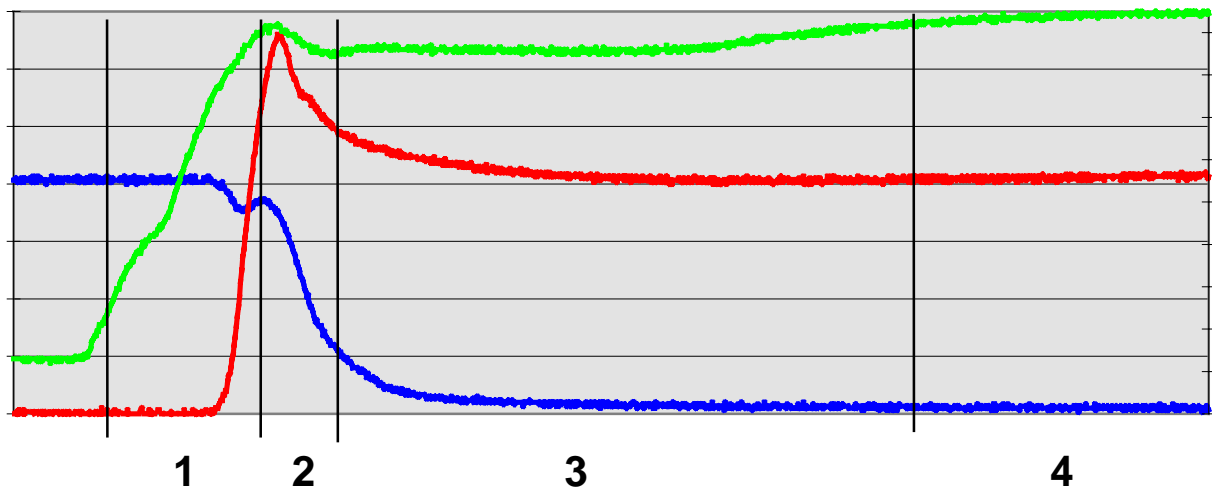By this measure the R_G and therefore the switching losses can remain on a low value.



range	determined by	condition	influenced by	influence on
1	$V_{GE} < V_{GEth}$	$C_{iss} = \text{const.}$	C'_{GE}	t_{don}
2	$V_{GEth} < V_{GE} < V_{GEM}$	$C_{iss} = \text{const.}$	C'_{GE}	di_C / dt
3	$V_{GE} = V_{GEM}$	$V_{GE} = \text{const.}$	R_G, C_{GC}	dV_{CE} / dt
4	$V_{GE} > V_{GEM}$	$C_{iss} = \text{const.}$	$C'_{GE} // C_{GC}$	dV_{CEsat} / dt

$$C'_{GE} = C_{GE} // C_G$$


For further information contact:

eupec
Marketing Department
Max Planck Str. 5
D-59581 Warstein


Tel: +49 2902 764-0
Fax: +49 2902-764-256
Internet: <http://www.eupec.com>
AN_CGE.doc

Example : FZ1200R33KF1, turn-on without C_G

V_{CE} : 500V / div, I_C : 600A / div

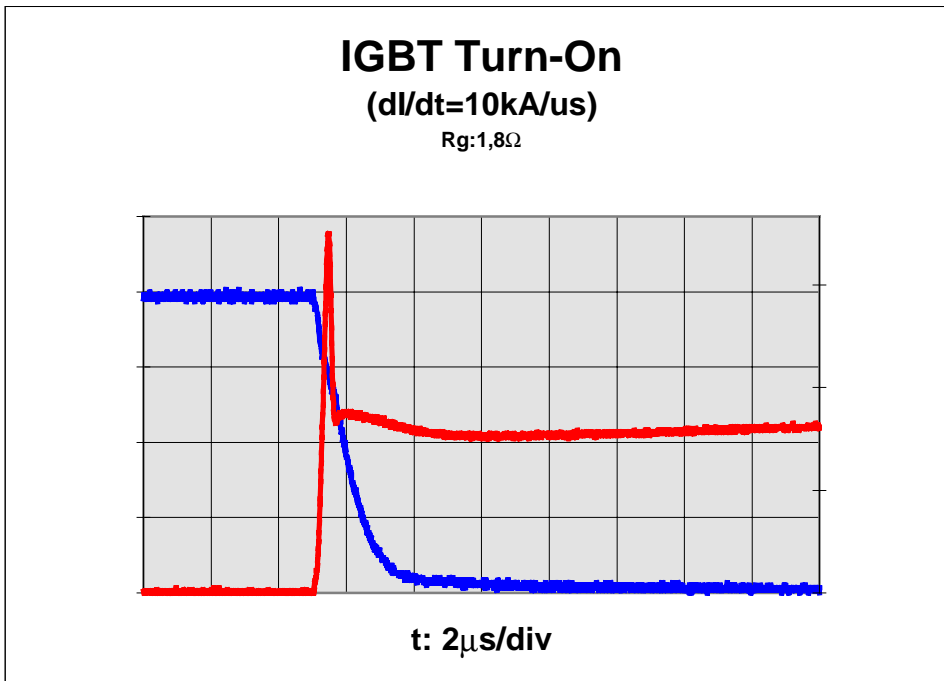

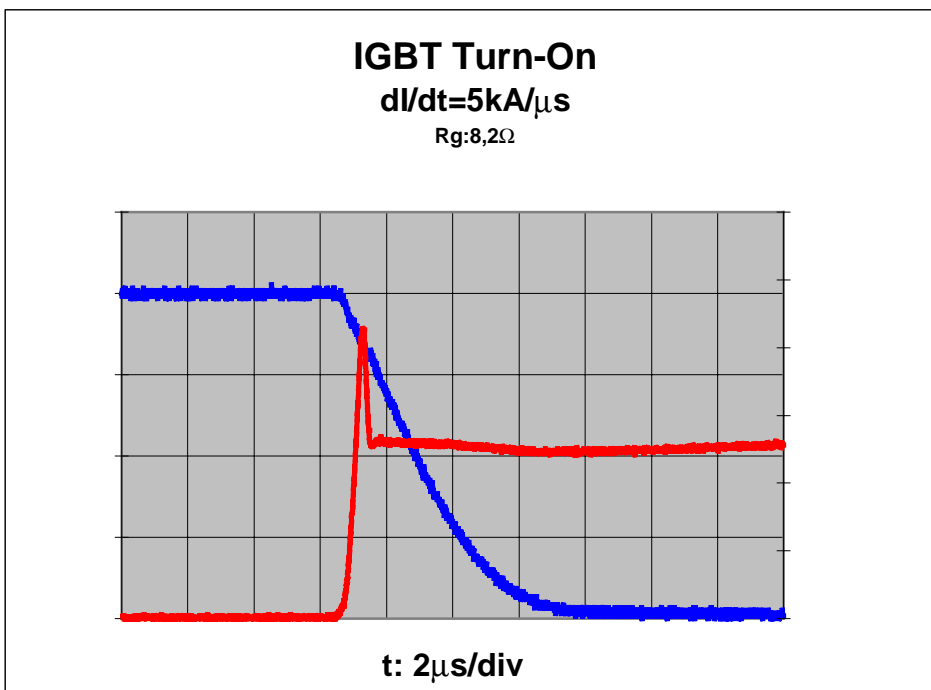high di_C/dt due to low gate resistor R_G



low dV_{CE}/dt and high turn-on losses due to high gate resistor R_G

For further information contact:

eupec

Marketing Department

Max Planck Str. 5

D-59581 Warstein

Tel: +49 2902 764-0


Fax: +49 2902-764-256

Internet: <http://www.eupec.com>

AN_CGE.doc

Solution:

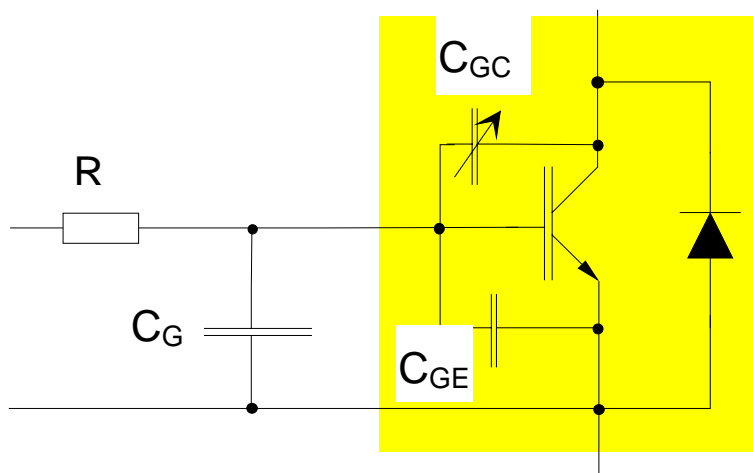An additional Capacitance between Gate & Emitter allows independent control of di_C/dt and dV_{CE}/dt



- dV_{CE}/dt is controlled via R_G and C_{GC}
- di_C/dt is controlled via R_G and $C_{GE} // C_G$

For further information contact:

eupec

Marketing Department

Max Planck Str. 5


D-59581 Warstein

Tel: +49 2902 764-0

Fax: +49 2902-764-256


Internet: <http://www.eupec.com>

AN_CGE.doc

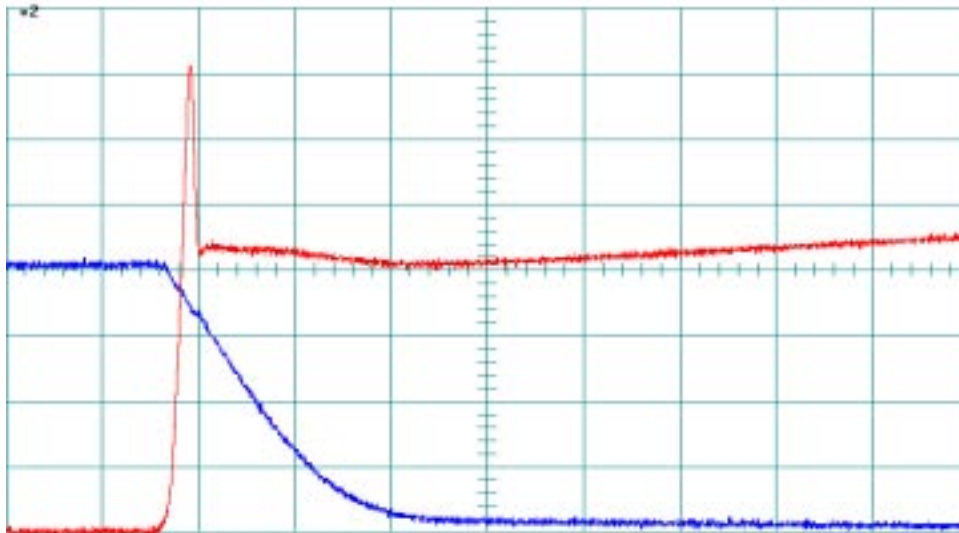


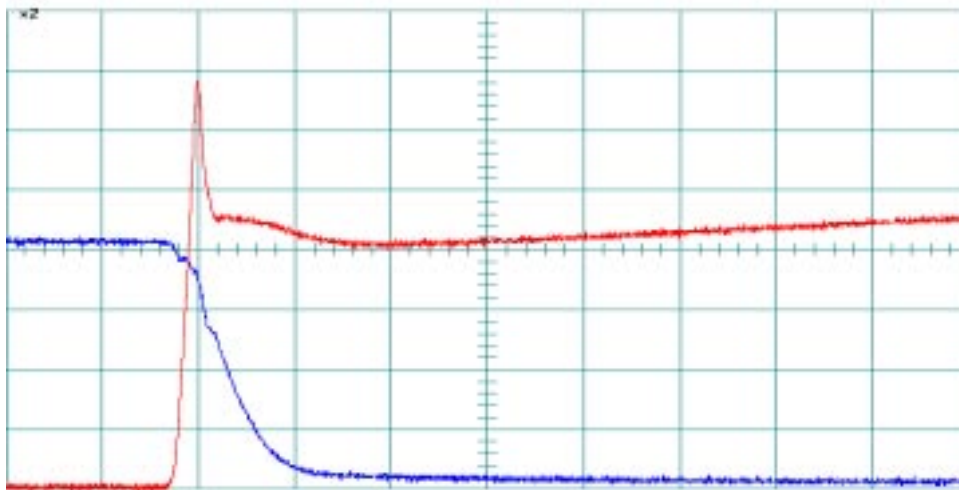Example:
FZ1200R33KF1
Variation of R_G and C_G

$R_G=8,2\Omega$, $C_G=0$, $I_C/dt= 5kA/\mu s$, $dV_{CE}/dt=0,6kV/\mu s$, $E_{on}=6,4J$



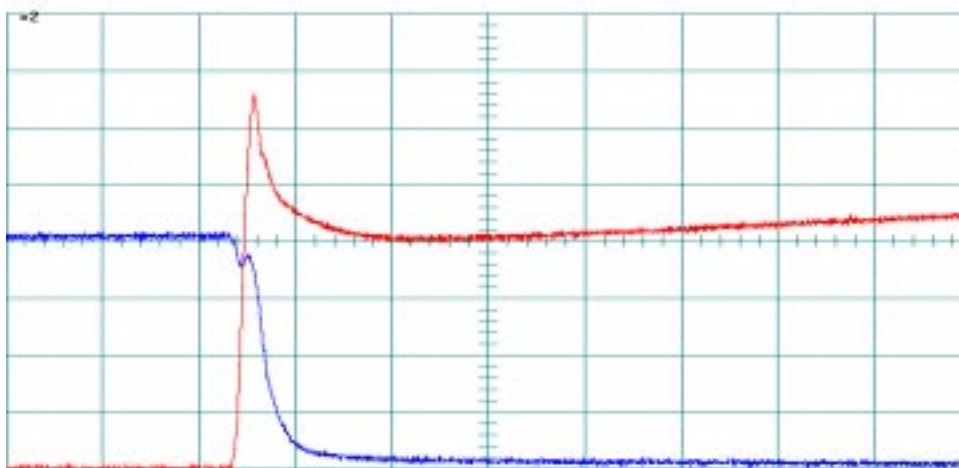$R_G=3,3\Omega$, $C_G=100nF$, $I_C/dt= 4,5kA/\mu s$, $dV_{CE}/dt=1kV/\mu s$, $E_{on}=4,1J$



$R_G=1,0\Omega$, $C_G=330nF$, $I_C/dt= 5,1kA/\mu s$, $dV_{CE}/dt=2,8kV/\mu s$, $E_{on}=2,8J$

For further information contact:

eupec

Marketing Department

Max Planck Str. 5

D-59581 Warstein

Tel: +49 2902 764-0

Fax: +49 2902-764-256

Internet: <http://www.eupec.com>

AN_CGE.doc